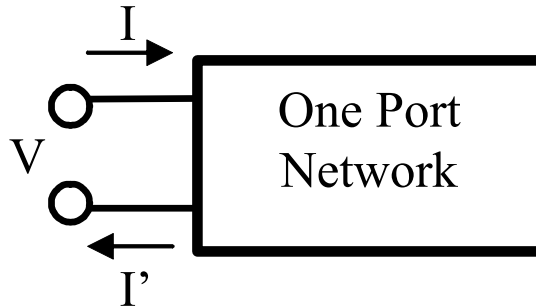


# Two-Port Networks


- One-port network:

$$V = Z \cdot I$$




$$I = I'$$

- Two-port network:

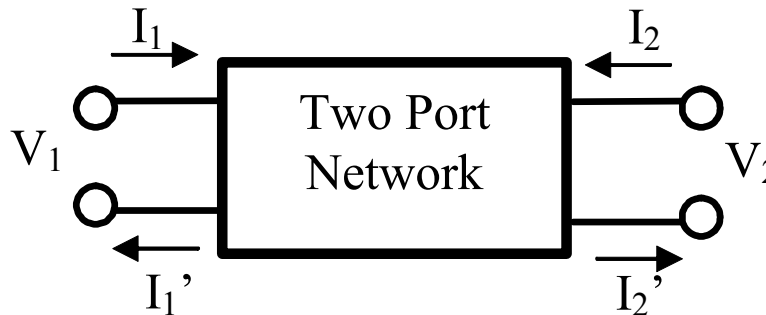

$$\begin{cases} I_1 = I_1' \\ I_2 = I_2' \end{cases}$$
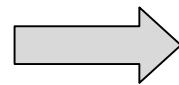
$$\begin{aligned} V_1 &= Z_{11} \cdot I_1 + Z_{12} \cdot I_2 \\ V_2 &= Z_{21} \cdot I_1 + Z_{22} \cdot I_2 \end{aligned}$$



$$[V] = [Z] \cdot [I]$$

# How to Determine Z Parameters?

$$\begin{aligned} V_1 &= Z_{11} \cdot I_1 + Z_{12} \cdot I_2 \\ V_2 &= Z_{21} \cdot I_1 + Z_{22} \cdot I_2 \end{aligned} \xrightarrow{I_2=0} \begin{aligned} Z_{11} &= \left. \frac{V_1}{I_1} \right|_{I_2=0} & Z_{21} &= \left. \frac{V_2}{I_1} \right|_{I_2=0} \end{aligned}$$

$$\xrightarrow{I_1=0} \begin{aligned} Z_{22} &= \left. \frac{V_2}{I_2} \right|_{I_1=0} & Z_{12} &= \left. \frac{V_1}{I_2} \right|_{I_1=0} \end{aligned}$$



Reciprocity:


$$Z_{12} = Z_{21}$$

# Y Parameters


$$[V] = [Z] \cdot [I] \quad \Rightarrow \quad [I] = [Z]^{-1} \cdot [V] \quad \Rightarrow \quad [Y] = [Z]^{-1}$$

$$\begin{aligned} I_1 &= Y_{11} \cdot V_1 + Y_{12} \cdot V_2 \\ I_2 &= Y_{21} \cdot V_1 + Y_{22} \cdot V_2 \end{aligned} \quad \xrightarrow{V_2=0} \quad \begin{aligned} Y_{11} &= \left. \frac{I_1}{V_1} \right|_{V_2=0} & Y_{21} &= \left. \frac{I_2}{V_1} \right|_{V_2=0} \end{aligned}$$


$$\xrightarrow{V_1=0} \quad \begin{aligned} Y_{22} &= \left. \frac{I_2}{V_2} \right|_{V_1=0} & Y_{12} &= \left. \frac{I_1}{V_2} \right|_{V_1=0} \end{aligned}$$

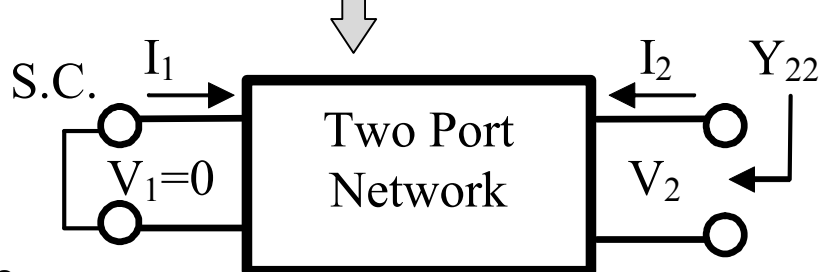

# Simple Networks

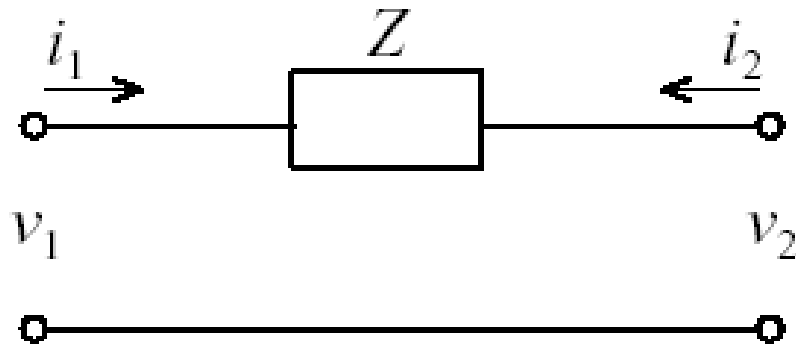


→  $[Z], [Y] - ???$

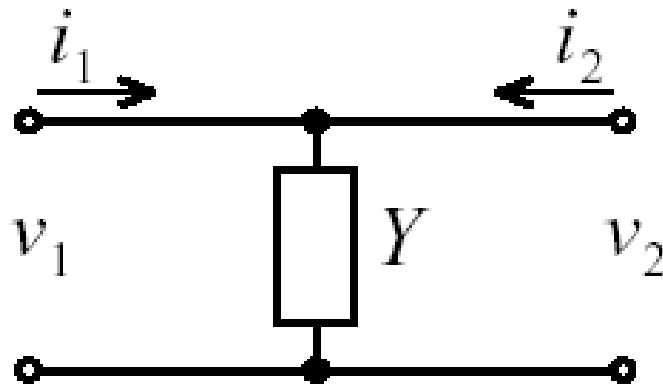

→  $[Z], [Y] - ???$


# Example: T-Network

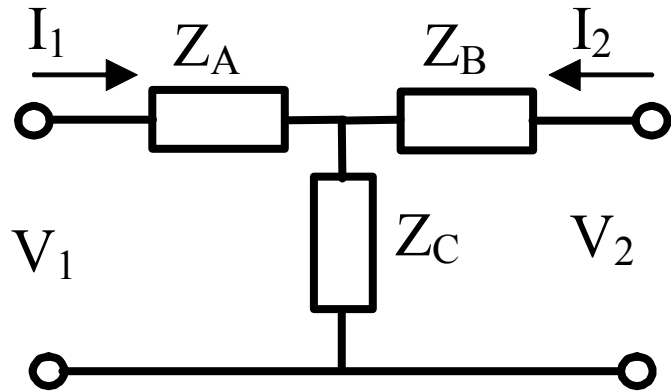


$$I_2 = 0 \rightarrow \begin{cases} Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = Z_A + Z_C \\ Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = Z_C \end{cases}$$

$$I_1 = 0 \rightarrow \begin{cases} Z_{12} = Z_{21} = Z_C \\ Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = Z_B + Z_C \end{cases}$$

# Example: Pi-Network

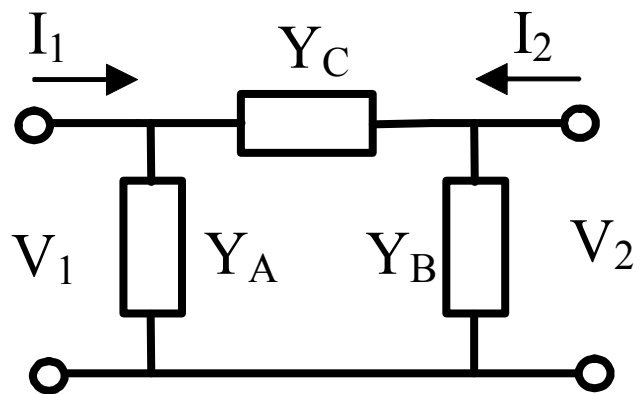


$$V_2 = 0$$

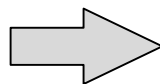

$$\begin{cases} Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = Y_A + Y_C \\ Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = -Y_C \end{cases}$$


$$V_1 = 0$$

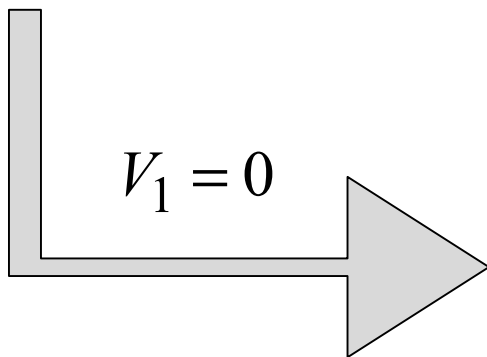





$$\begin{cases} Y_{12} = Y_{21} = -Y_C \\ Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = Y_B + Y_C \end{cases}$$
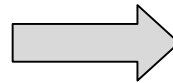
# ABCD Parameters


$$\begin{aligned} V_1 &= A \cdot V_2 + B \cdot I_2 \\ I_1 &= C \cdot V_2 + D \cdot I_2 \end{aligned}$$


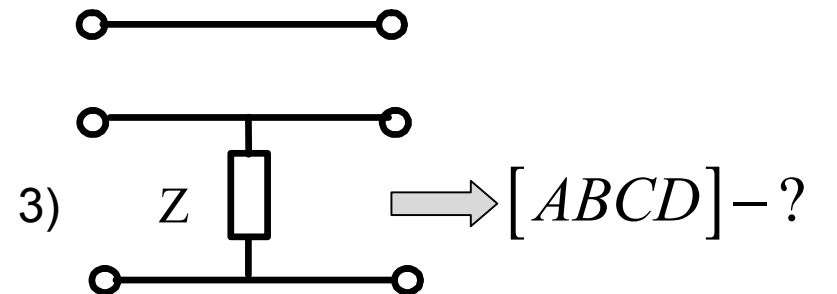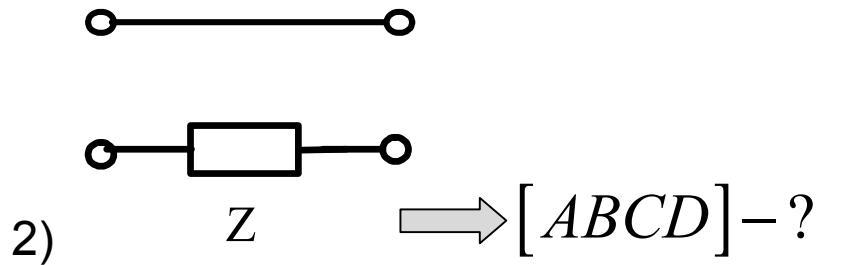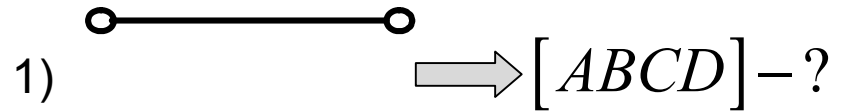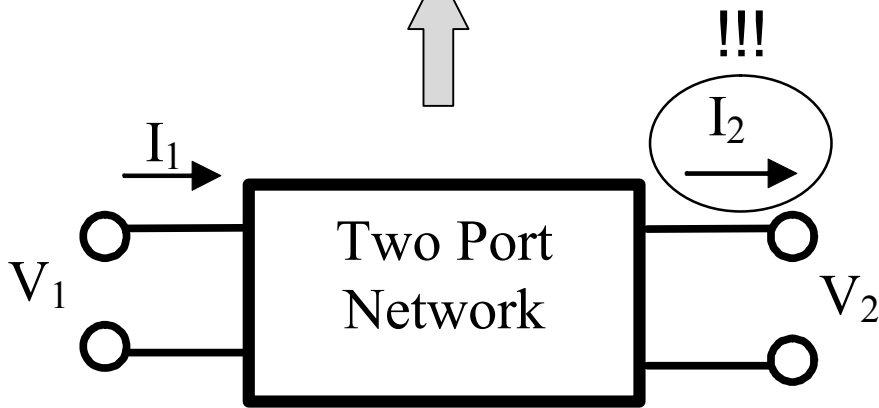
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \cdot \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$



# ABCD Parameters of TL

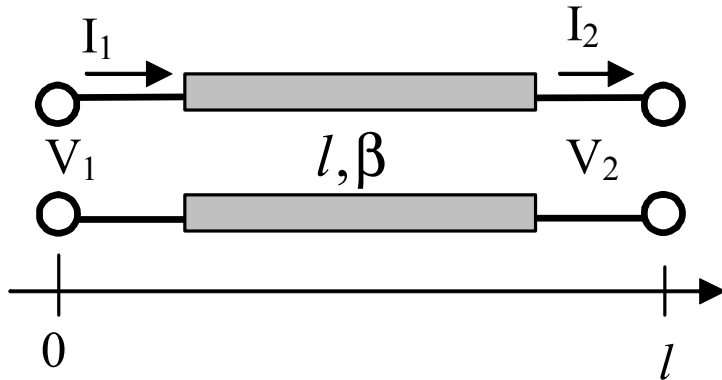


$$\left\{ \begin{array}{l} V_1 = V^+ + V^-, \quad I_1 = \frac{1}{Z_0} (V^+ - V^-) \\ V_2 = V^+ e^{-j\beta l} + V^- e^{j\beta l} \\ I_2 = \frac{1}{Z_0} (V^+ e^{-j\beta l} - V^- e^{j\beta l}) \end{array} \right.$$


$$\left\{ \begin{array}{l} V_2 = V_1 \cos \beta l + jI_1 Z_0 \sin \beta l \\ I_2 = j \frac{V_1}{Z_0} \sin \beta l + I_1 \cos \beta l \end{array} \right. \Rightarrow [ABCD] = \begin{bmatrix} \cos \beta l & jZ_0 \sin \beta l \\ jY_0 \sin \beta l & \cos \beta l \end{bmatrix}$$



# Series Connection of Two-Port Networks


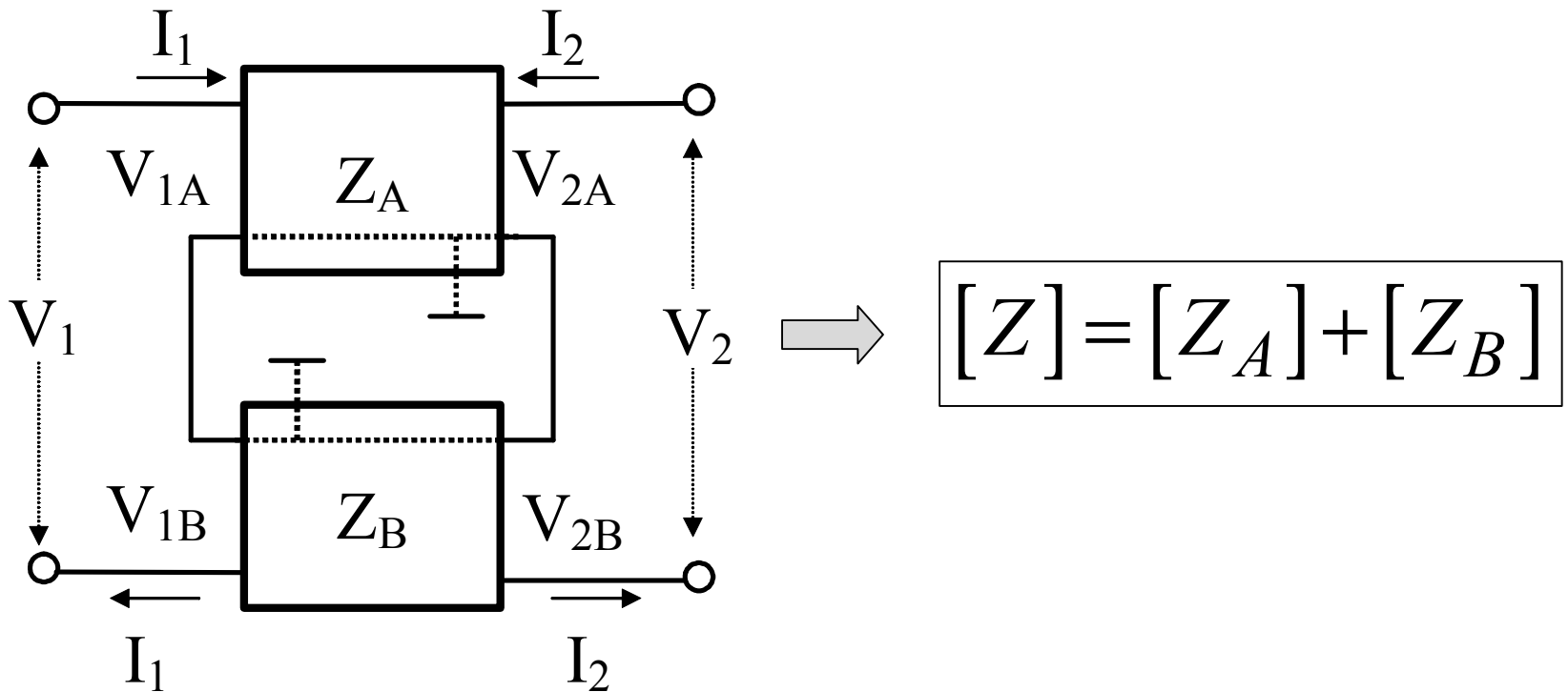

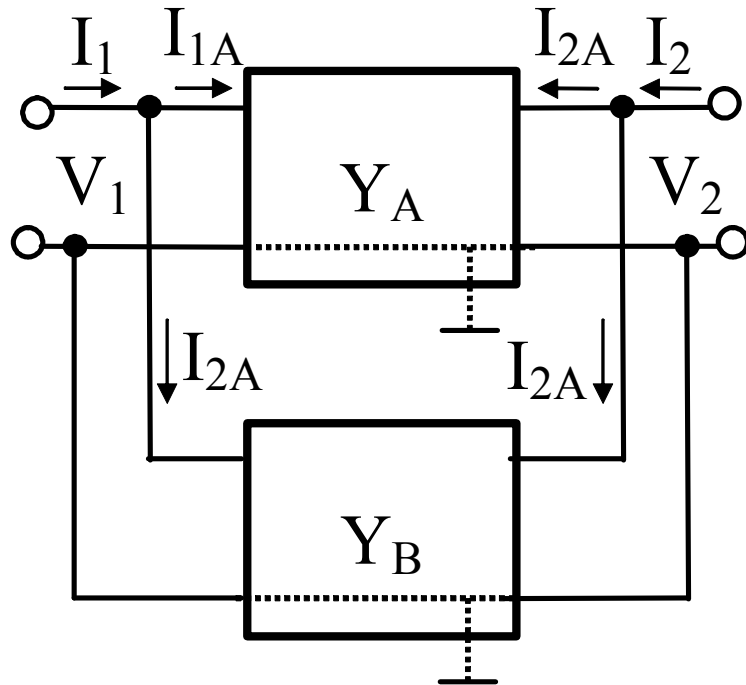
# Parallel Connection of Two-Port Networks



$$[Y] = [Y_A] + [Y_B]$$
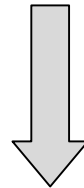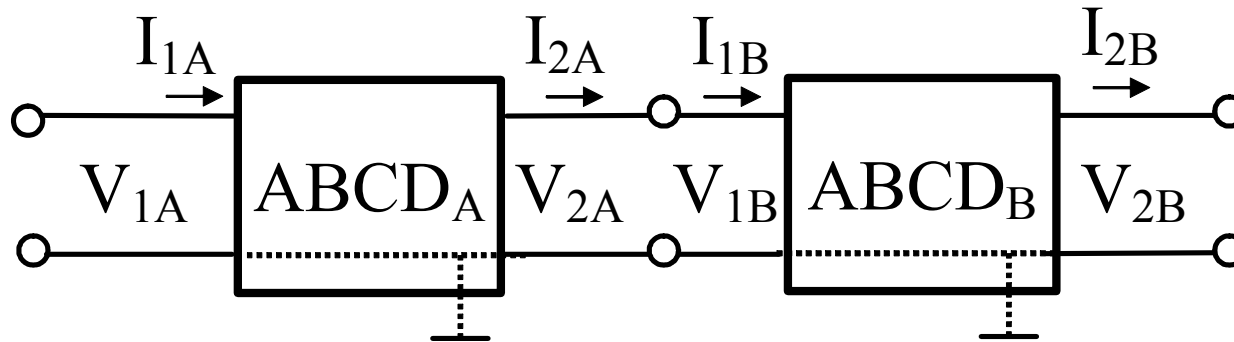
# Cascade Connection of Two-Port Networks



$$\boxed{[ABCD] = [ABCD_A] + [ABCD_B]}$$